

Amplifier circuit so that a GPIO-generated signal from your Raspberry Pi is boosted by the TSH82 op amp and then sent to a piezo transducer (speaker).

Components

- Raspberry Pi 4B (with the GPIO header available)
- TSH82 Dual Operational Amplifier
- Breadboard (for prototyping)
- Jumper Wires
- Resistors:
 - One $10\text{ k}\Omega$ resistor (for feedback from the inverting input to ground)
 - One $100\text{ k}\Omega$ resistor (for feedback from the op amp output to the inverting input)
- Piezo Transducer (Speaker)
- Power Supply: You can use the Raspberry Pi's 5V and Ground pins

Step-by-Step Wiring Instructions

1. Connect the Raspberry Pi to the Op Amp (Non-Inverting Input)

- GPIO Signal to Non-Inverting Input (+):
 - Choose a GPIO pin to generate your audio signal (for example, GPIO18 which is available on physical Pin 12).
 - Run a jumper wire from this GPIO pin directly to the non-inverting (+) input of the TSH82 op amp.
 - Tip: On the op amp, there may be a pair of parallel pads for the non-inverting input; use the one that is marked as “+” or “non-inverting.”

2. Mount the TSH82 on a Breadboard

- Carefully insert the TSH82 into the breadboard so that you can easily connect jumper wires to its pins.
- Ensure that the op amp's pins are accessible for wiring the inputs, outputs, power, and feedback network.

3. Establish the Signal Connection

- Direct Connection:

- Use a jumper wire to connect the op amp's non-inverting input (+) (from step 1) to the corresponding breadboard row where your GPIO signal is available.

4. Set Up the Feedback Network with the Resistors

- Feedback Resistor (R2 – 100 kΩ):

- Connect one end of the 100 kΩ resistor to the op amp's output pin.

- Connect the other end of this resistor to the inverting input (–) of the op amp.

- Ground Resistor (R1 – 10 kΩ):

- Connect one end of the 10 kΩ resistor to the same inverting input (–) of the op amp (where R2 is already connected).

- Connect the other end of the 10 kΩ resistor to the breadboard's ground rail.

This resistor network sets the amplifier's gain using the formula:

$$\text{Gain } A = 1 + \{R2\}/\{R1\}$$

For R2 = 100 kΩ and R1 = 10 kΩ, Gain ≈ 11.

5. Establish a Common Ground

- Connect a ground pin from your Raspberry Pi (for example, Pin 6) to the ground rail on your breadboard.
- Make sure that all components (the op amp and the piezo transducer) share this common ground.


6. Connect Power to the Breadboard


- VCC Connection:
 - Connect the Raspberry Pi's 5V pin (e.g., Pin 2 or Pin 4) to the positive power rail on the breadboard.
- Ground Connection:
 - Also, ensure that the ground from the Raspberry Pi is connected to the breadboard's ground rail.
 - Then, wire the TSH82's VCC (positive power pin) to the breadboard's positive rail and its -VEE (negative supply) to the ground rail.
 - In a single-supply configuration (which we're using here), the -VEE is tied to ground.

7. Connect the Op Amp Output to the Piezo Transducer

- Output Connection:
 - Run a jumper wire from the op amp's output to the positive (+) terminal of the piezo transducer.
- Transducer Ground:
 - Connect the negative (-) terminal of the piezo transducer to the breadboard's ground rail.

Visual Summary (Simplified Schematic)

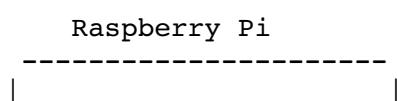

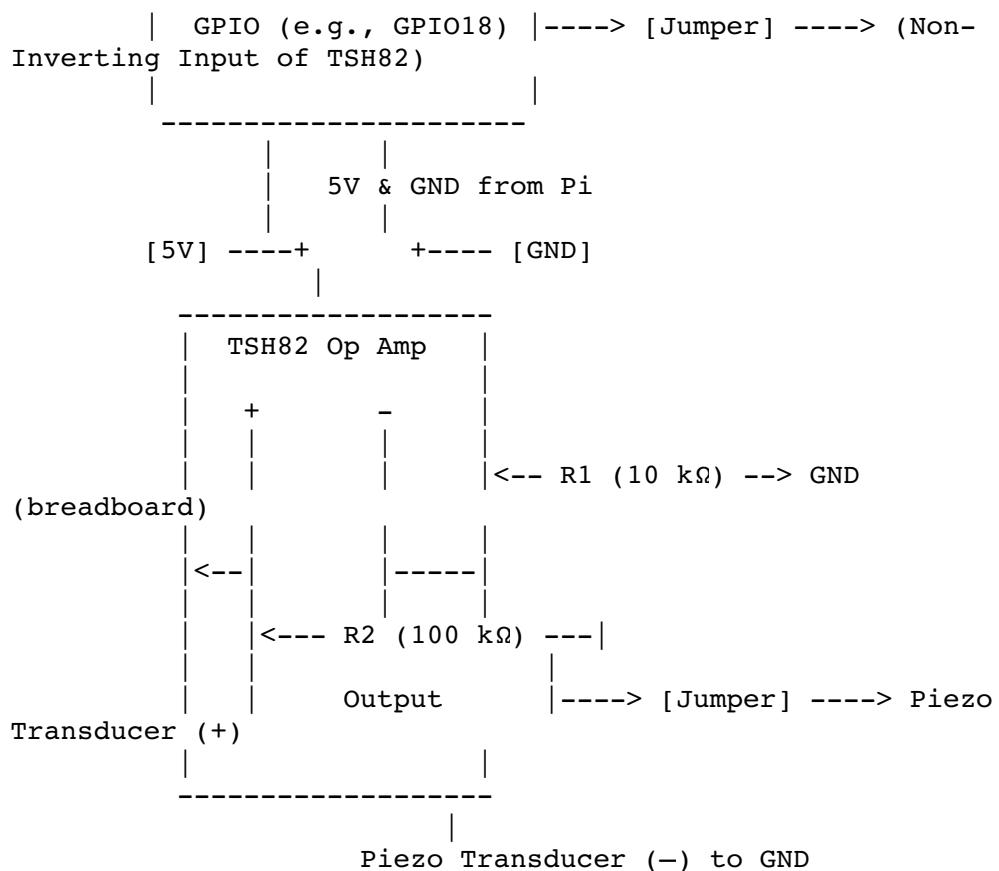

Note: The op amp's VCC and –VEE should be connected to the breadboard's 5V and Ground rails, respectively.

Given Below is the connection I made

This will be useful for reference

